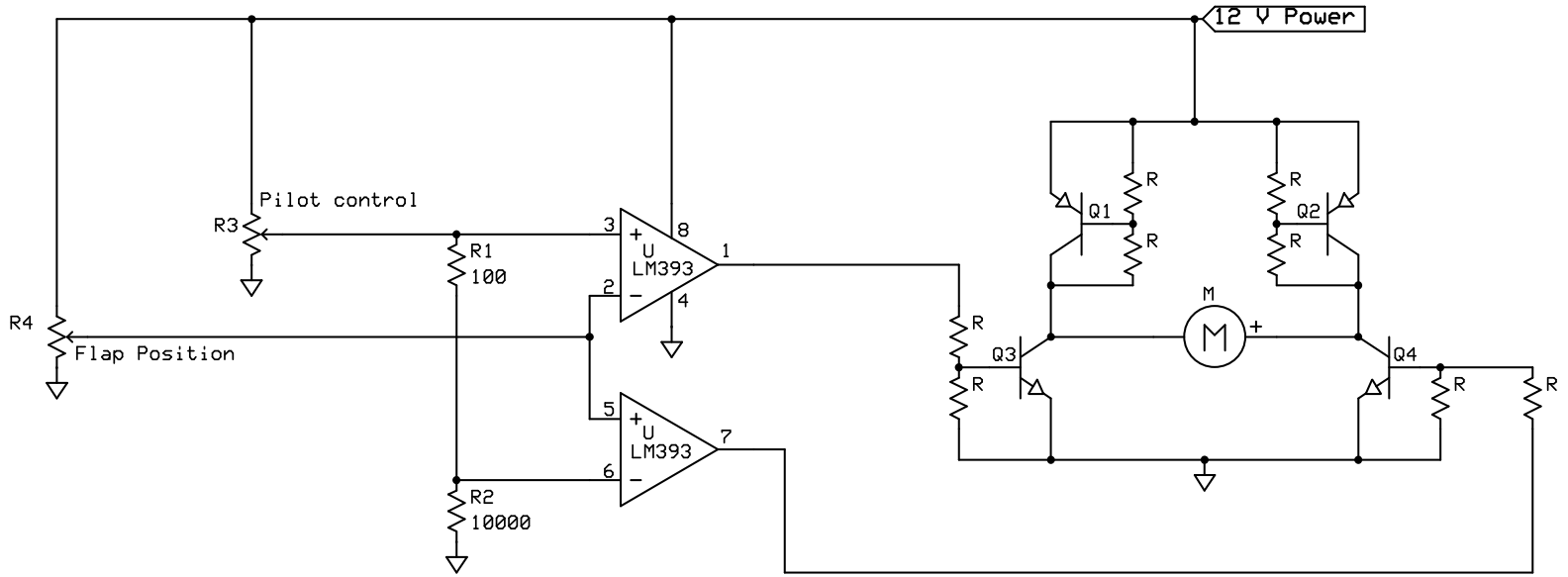
Use two electrically similar potentiometers(volume controls), one controlled by the pilot, and the other connected to the flap system. When they do not agree, the motor runs.



MorningStar Software, Inc.		
Simple Flap Preset Control		
Designer's name	Rev 1.0 5/29/2011	Page # or name